ELECTRICAL ENGINEERING

Time: 3 hours

Full Marks: 200

5

5

080097

Instructions :

- (1) Answer Question No. 1 which is compulsory and any nine from the rest.
- (2) The figures in the margin indicate full marks for the questions.
- 1. (a) Determine the current in 20 Ω resistor of the network shown in Fig. 1 using Thevenin's theorem :





(b) Find the transfer function G(s) = X(s) / F(s) for the translational mechanical network shown in Fig. 2 :

 $2 \text{ N-s/m} \qquad 5 \text{ N/m} \qquad 5 \text{ N/m} \qquad 5 \text{ K} \qquad 5 \text{ K$



(c) State three differences between RTD and thermistor. 3

- (d) The potential field is given as $V = 2x^2y 5z$. Find at point P(-4, 3, 6), the potential (V), the electric field intensity (E) with its direction and the electric flux density (D).
- (e) State two differences between lap winding and wave winding.

11/ELECT ENGG

1

[P.T.O.

4

2. (a) Use mesh current analysis to find the voltage V_x across the current source of Fig. 3 :



(b) A balanced 3-phase star-connected load of 120 kW takes a leading current of 100 A when connected across a 3-phase, 3.3 kV, 50 Hz supply. Determine the impedance, resistance, capacitance and power factor of the load.

2

5

2

7

(c) Determine the time constant of the circuit shown in Fig. 4 :



Fig. 4

(d) A 10 mH coil in series with a loss-free capacitor is connected to a variable frequency source which supplies a constant voltage of 10 V. The circuit has a maximum value of 0.1 A at a frequency of 80 kHz. Calculate (i) the capacitance of the capacitor and (ii) the Q-factor of the coil and the half-power frequencies.

3. (a) State maximum power transfer theorem in an a.c. network.

(b) The resonant frequency of the tuned circuit shown in Fig. 5 is 1000 rad/s. Calculate the self-inductances of the two coils and critical value of mutual inductance :



2

11/ELECT ENGG

14.

11/

13. (a

(b



- (b) What is meant by back e.m.f. in a d.c. motor? Derive the torque equation of a d.c. motor.
- (c) A separately excited d.c. motor has an armature resistance of 0.5Ω . It runs on a 250 V d.c. supply drawing an armature current of 20 A at 1500 r.p.m. Find the torque developed for armature current of 10 A for same field current.
- (d) A 3-phase star-connected alternator is rated at 1600 kVA, 13.5 kV. The armature effective resistance and synchronous reactance are 1.5Ω /phase and 30 Ω /phase respectively. Calculate the percentage voltage regulation for a load of 1280 kW at 0.8 leading power factor.
- 5. (a) The open-loop transfer function of a control system is given by

$$G(s) = \frac{2 \cdot 5K}{s(0 \cdot 4s + 1)(0 \cdot 2s + 1)}$$

- (i) Sketch the Nyquist plot to determine phase crossover frequency and gain margin.
- (ii) Determine phase margin for K = 3.

11/ELECT ENGG

3

[P.T.O.

12

6

5

(b) If the potential coil of a wattmeter is subjected to a voltage v(t) and current coil to a current i(t) as given below, find the power read by the wattmeter :

5

:

 $v(t) = 10 + 5 \sin (\omega t + 45^\circ) + 3 \sin (2\omega t + 30^\circ)$ $i(t) = 5 + 4 \sin (2\omega t - 30^\circ) + 3 \sin (\omega t + 45^\circ)$

- (c) A 400 W carrier is modulated to a depth of 75 percent. Calculate the total power in the modulated wave. Assume the modulating signal to be sinusoidal.
- **6.** (a) Define commutation. With neat diagrams, explain the process of commutation in d.c. generators.
 - (b) The open-loop transfer function of a system is given as

$$G(s)H(s) = \frac{s+1}{(s+4)(s^2+5s+k)}$$

Find the value of k such that the system has a zero steady-state error for a step input.

- (c) What is strain gauge? Derive an expression for gauge factor in terms of Poisson's ratio.
- (d) An op-amp, having a slew rate of $31 \cdot 4 \text{ V}/\mu \text{s}$, is connected in a voltage follower configuration. If the input voltage $V_i = 0.5 \sin \omega t$, then find the minimum frequency at which the slew rate limited distortion would set in the output.
- 7. (a) Find the output voltage (V_o) for the circuit shown in Fig. 7 for an input voltage $V_i = 5 \sin 100\pi t$:



Fig. 7

11/ELECT ENGG

1

1:

- (b) What would happen if a d.c. motor is directly switched on to the supply without any starter and why?
- (c) Find the transfer function relating the capacitor voltage, $V_o(s)$ to the input voltage $E_i(s)$ of the circuit shown in Fig. 8 and if a step input is applied, then find the maximum overshoot in the output V_o of the circuit :



- (d) Why is Maxwell bridge limited to the measurement of medium-Q coils?
- **8.** (a) With a neat diagram, explain the principle, working and construction of a PMMC instrument.
 - (b) What happens when an ammeter is connected across a circuit and why?
 - (c) Define the bandwidth of the BJT amplifier.
 - (d) The speed regulation of two 500 kW alternators A and B running in parallel are 100% to 104% and 100% to 105% from full-load to no-load respectively. How will the two alternators share a load of 800 kW? Find the load at which one machine ceases to supply any portion of the load.
- 9. (a) A unity feedback system has open-loop transfer function

$$G(s) = \frac{K(s+5)}{s(s+2)}; \quad K \ge 0$$

- (i) Draw a rough sketch of root locus plot such that the complex roots of the characteristic equation move along a circle.
- (ii) As K increases, does the system become stable? Justify your answer.
- (iii) Find the value of K (if it exists) so that the damping ratio of complex closed poles is 0.3. 15

11/ELECT ENGG

5

[P.T.O.

6

4

8

4

2

6

- (b) With a neat labelled diagram, describe the working of a 4-point d.c. shunt motor starter.
- 10. (a) The line-to-line voltage of a 3-phase, 50 Hz, a.c. circuit shown in Fig. 9 is 100 V. Assuming that the phase sequence is *RYB*, find the wattmeter readings W_1 and W_2 :





(b) Find the quiescent collector voltage for the circuit shown in Fig. 10. Assume $V_{BE} = 0.7$ V and $V_{CE, \text{ saturation}} = 0.2$ V :



11/ELECT ENGG

6

ODVA TOALNA LE

414 1. C. C.

5

6

- (c) Which d.c. motor is more suitable for traction purpose and why?
- (d) Write three mechanical and four electrical instruments/devices used for the measurement of flow rate.
- 11. (a) Derive the general wave equations for the transmission line.
 - (b) Two semi-infinite conducting sheets are placed at right angles to each other. A point charge Q is placed at a perpendicular distance d from both sheets. Find the net force on the charge Q.
 - (c) The open-loop transfer function of a unity feedback system is

$$G(s) = \frac{K(s+1)}{s^3 + \beta s^2 + 2s + 1}$$

Determine the constant K and β for which the system oscillates at 2 rad/s.

- (d) The current passing through a resistor of $(100\pm 2) \Omega$ is $(2\cdot 00\pm 0\cdot 001)$ A. Calculate the limiting error in the computed value of power dissipation.
- **12.** (a) The open-loop transfer function of a unity feedback control system is given by

$$G(s) = \frac{25}{s(s+5)}$$

- (i) Calculate the natural frequency of oscillations, damped frequency of oscillations, damping factor, damping ratio and the maximum overshoot for a unit-step input.
- (ii) Calculate the steady-state error for unit-ramp input.
- (iii) If the damping ratio is to be made 0.75 using a tachometer feedback, calculate the tachometer constant and determine the maximum overshoot.
- (b) Show that the resonant frequency of a series *RLC* circuit is the geometric mean of the lower- and upper-half power frequencies.

11/ELECT ENGG

[P.T.O.

5

5

3

6

6

13. (a) Determine the time taken for a step response to reach 98% of the final value of a system given by

$$G(s) = \frac{4}{(s+1)}$$

(b) Determine the load impedance Z_L so that maximum power transfer takes place from the source to the load of Fig. 11. Also determine the maximum power.



Fig. 11

- (c) What is regenerative breaking in d.c. motor?
- (d) The sum of products form of a Boolean function is $\Sigma(0, 1, 3, 7, 11)$, where the inputs are A, B, C, D (A is MSB and D is LSB). Draw the Karnaugh map and find the equivalent minimize expression of the function.
- 14. (a) Draw a circuit using maximum of five gates (AND, OR and NOT) to realize the function $F = \overline{XY} + YZ$, taking X, Y and Z as input.
 - (b) Write four differences between microprocessor and microcontroller.
 - (c) What are bistable multivibrators? Write the names of two multivibrators with its truth table.
 - (d) Draw the energy band diagrams of biased and unbiased *p*-*n* junction.

11/ELECT ENGG

YY8-262

SEAL

6

6

3

5

7

4

5