SUBJECT: ELECTRONICS/ TELECOMMUNICATION ENGINEERING: PAPER – 2 SET-A

Time: 3 hours

Full Marks: 200

Note: Answer Question No. 1 and any four from the rest. All questions carry equal marks.

1. Attempt any 10 (ten).

 $10 \times 4 = 40$

- (a) State how a non-symmetrical square wave can be generated using a comparator circuit.
- (b) How will you draw the d.c. load line on the output characteristics of a transistor?
- (c) Why is peak inverse voltage important in diode rectifier operations?
- (d) What do you mean by a cyclic code? Give an example of a cyclic code.
- (e) What do you mean by two-level logic? What is its main advantage?
- (f) Define clock skew and time race in sequential circuits.
- (g) What is the characteristic impedance of a transmission line? Draw the RF equivalent circuit representation of a transmission line.
- (h) Explain Y, I and Q signals in color television.
- (i) Distinguish between velocity and current modulations in the klystron amplifier.
- (j) Describe the operation of the track-while-scan radar.
- (k) Define entropy in information theory and give its mathematical expression.
- (1) Define maximum frequency deviation in frequency modulation. How is it used to classify a signal into either a narrowband or a wideband frequency modulated signal?
- 2. Attempt any 8 (eight).

8×5=40

- (a) Explain the principle of operation of fixed bias and self bias circuits using bipolar junction transistor in common emitter configuration.
- (b) Determine R_C and R_B for fixed biasing circuit of a common emitter transistor if $V_{CC} = 12V$, $\beta = 50$, I_C (Q) = 2.35 mA, and V_{CE} (Q) = 6.83V.

- (c) A 4-bit number is represented by ABCD with D as the LSB. Design a logic circuit that will produce a 1 whenever the input is greater than 0010 but less than 1000. Use minimum number of gates.
- (d) Design an 8:1 multiplexer from a minimum number of 4:1 multiplexers.
- (e) Explain Gain margin and Phase margin from the Nyquist plot.
- (f) A unity feedback system has an open-loop transfer function

$$G(s) = \frac{10(s+1)}{s(s+2)(s+5)}$$

Determine the steady-state error for r(t) = 3 + 10t.

- (g) A 10 MHz carrier is frequency modulated using a modulating signal $e_m = E_m \sin 10^3 \pi t$. The resultant signal has a frequency deviation of 5 kHz. Calculate the modulation index and bandwidth of the modulated signal.
- (h) Explain low and high level modulations in amplitude modulation.
- (i) A microwave signal of 9.2 GHz is propagating in dominant mode through a rectangular waveguide filled with air. If inside dimensions of the waveguide are 2 cm × 1 cm, calculate
 - i) the cut-off frequency.
 - ii) the guide wavelength.
- (j) Draw a sketch of electromagnetic wavefronts incident at an angle on a perfectly conducting plane surface.
- 3. Attempt any 5 (five).

5×8=40

- (a) Draw two input OR gate and AND gate circuits using diodes and other components and explain their operations assuming approximate equivalent models for the diodes.
- (b) Determine the value of gain K and velocity feedback constant k_v in Fig. 3 (b) so that the maximum overshoot in the unit step response is 0.2 and the peak time is 1 sec.



- (c) Draw the block diagram of filtering method for generating a single sideband suppressed carrier modulated signal for an audio baseband signal. What are the frequency requirements of the filter used for generation of the modulated signal?
- (d) Draw the block diagram of monochrome TV transmitter and explain in brief the functioning of the video amplifier and sound transmitter blocks.
- (e) A reflex klystron is to be amplitude modulated only. Draw the necessary circuit diagram with the klystron to produce such modulation.
- (f) A unity feedback system has a forward loop transfer function:

$$G(s) = \frac{K}{(s+1)^3(s+4)}$$

Determine:

- i) the range of K for closed –loop system stability.
- ii) the frequency of oscillations when the system is marginally stable.
- (g) Draw the current mirror circuit using two back-to-back n-p-n transistors and write the equation of the mirror current from the circuit.
- **4.** Attempt any 4 (four).

4×10=40

- (a) Consider a discrete memoryless source with source alphabets $\{S_0, S_1, S_2,\}$ and corresponding source probabilities $P(s_0) = 0.7$, $P(s_1) = 0.15$, and $P(s_2) = 0.15$. Calculate:
 - i) the entropy of the source.
 - ii) the entropy of second order extension of the source.

(b) Consider a feedback system with the characteristic equation

$$1 + \frac{K}{s(s+1)(s+2)} = 0$$

Compute the angles of asymptotes of the root-locus branches with the real axis of the splane. Also find the centroid and the breakaway points of the root-locus of the system. Assume that *K* varies from 0 to ∞ .

(c) Consider a third order system with the characteristic equation $s^3 + 3408.3 s^2 + 1.204 \times 10^6 s + 1.5 \times 10^7 K = 0$. Find the critical value of K for

stability using Routh-Hurwitz criterion.

- (d) Explain the following parameters used to characterize a directional coupler:
 - i) Coupling coefficient.
 - ii) Directivity of an ideal directional coupler.
- (e) A slotted line is terminated by different types of microwave loads. Draw the voltage standing wave within a rectangular waveguide when it is terminated by
 - i) sorted load
 - ii) matched load

Also determine the VSWRs for the sorted and matched loads.

5. Attempt any 2 (two).

2×20=40

- (a) Discuss similarities and differences of the two major television systems of the world with respect to their standards required for transmission and reception.
- (b) Describe the coherent detection process of double sideband suppressed carrier modulated signal and plot the spectrum of the detected signal.
- (c) Give the schematic of a Magic Tee used in microwave measurements. Obtain the S parameters of the Magic Tee.

6. Attempt any 4 (four).

(a) Draw the bipolar junction transistor circuit for the common emitter configuration. Sketch the output characteristics of the circuit and hence indicate the active, saturation and cut-off regions on it.

4×10=40

- (b) Draw different stages of a typical operational amplifier and briefly explain functioning of each stage.
- (c) Show that the negative feedback improves the gain stability of an amplifier.
- (d) Determine the truth table of a 3-line to 8-line decoder and draw the corresponding logic circuit.
- (e) With the help of a state diagram, design and implement a BCD counter using J-K Flip-Flops.
- 7. Attempt any 2 (two).

$2 \times 20 = 40$

(a) Draw the free-body diagram of the mechanical system shown in Fig. 7 (a) and write the force equation. What is the transfer function of the system? Write the parameters of an electrical system analogous to the above mechanical system using the Force-Current Analogy.



- (b) Explain the different types of errors in Delta modulator? How can these be removed? Explain with relevant diagrams.
- (c) A non-inverting op-amp has got a gain of 10. The open-loop gain of the op-amp is $2 \times$ 10⁵. The output resistance of the op-amp without feedback is 75 Ω . Draw the circuit diagram of the non-inverting amplifier and calculate the output resistance with feedback.